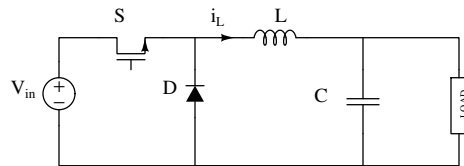



EE3203: Power Electronics

Tutorial 2


1. A step down converter is operating with the following parameters. $V_{in} = 30\text{ V}$ and $T_s = 1000\mu\text{s}$ and $T_{ON} = 125\mu\text{s}$. Find
 - (a) The steady state output voltage of the converter (Assume sufficiently large filter elements are present and the switches are ideal)
 - (b) The steady state current flowing through the inductor, if a load of $R = 5\Omega$ is connected at the output of the converter.



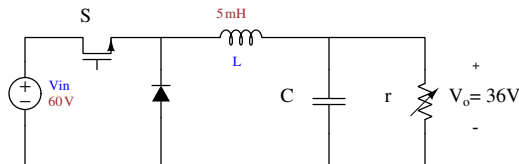
2. Find the range of duty ratio for a step down converter operating in figure 1 at $f_s = 50\text{ kHz}$ when the input voltage varies from 30 V to 70 V keeping the output voltage at 15 V .
3. A buck converter is operating with an input voltage $V_{in} = 60\text{ V}$, switching frequency $f_s = 50\text{ kHz}$, duty ratio of the switch $d = 0.25$. The filter inductance and capacitance are $L = 10\text{ mH}$ and $C = 100\mu\text{F}$ respectively. For a load of $R = 5\Omega$ find
 - (a) Steady state output voltage across the load and current through the load
 - (b) Ripple current in the inductor expressed as a fraction of output dc current
 - (c) Energy stored in the inductor in one switching cycle
 - (d) Ripple voltage in the capacitor expressed as a fraction of output dc voltage
 - (e) Energy stored in the capacitor in one switching cycle
4. A buck converter feeding a variable resistance load. The converter is operating at a switching frequency of $f_s = 100\text{ kHz}$ and duty ratio $d = 0.6$, filter inductance $L = 5\text{ mH}$. The output voltage is 36 V while the input is 60 V . Assuming all ideal components and the output to be ripple free, find the value of the load resistance such that the inductor current is just continuous.



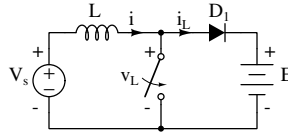5. A boost converter has an average voltage of $V_a = 15\text{ V}$ for an input voltage of $V_s = 5\text{ V}$. The average load current is $I_a = 0.5\text{ A}$. The switching frequency is 25 kHz . If $L = 150\text{ }\mu\text{H}$ and $C = 220\text{ }\mu\text{F}$, determine
- Duty cycle, d
 - Ripple current of the inductor, ΔI
 - Peak current of the inductor, I_L
 - Ripple voltage of the filter capacitor, ΔV
 - Critical values of L and C
6. The dc-dc converter shown is used to control power flow from a dc voltage, $V_s = 110\text{ V}$ to a battery voltage, $E = 220\text{ V}$. The power transferred to the battery is 30 kW . The current ripple of the inductor is negligible. Determine:
- Duty cycle, d
 - Effective load resistance, R_{eq}
 - Average input current, I_s



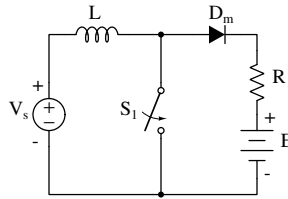7. For the problem 6, plot the instantaneous inductor current and current through the battery, E if the inductor L has a finite value of $L = 7.5\text{ mH}$, $f = 250\text{ Hz}$ and $d = 0.5$.
8. The boost converter shown has $R = 10\text{ }\Omega$, $L = 6.5\text{ mH}$, $E = 5\text{ V}$ and $d = 0.5$. Find I_1 , I_2 and ΔI .



9. In a buck-boost converter, consider all components to be ideal. Let V_s vary between 8 V to 40 V , $V_o = 15\text{ V}$, $f_s = 20\text{ kHz}$ and $C = 470\text{ }\mu\text{F}$. Calculate L_{min} that will keep the converter operating in continuous conduction mode if $P_o \geq 2\text{ W}$.
10. In a buck-boost converter, $V_s = 12\text{ V}$, $V_o = 1\text{ V}$, $I_o = 250\text{ mA}$, $L = 150\text{ }\mu\text{H}$, $C = 470\text{ }\mu\text{F}$, and $f_s = 20\text{ kHz}$. Calculate ΔV_o (peak-peak).
11. Calculate the rms value of the ripple current in problem 10 through diode and, hence, through the capacitor.

12. In a buck-boost converter operating at 20 kHz , $L = 0.05\text{ mH}$. The output capacitor C is sufficiently large and $V_s = 15\text{ V}$. The output is to be regulated at 10 V and the converter is supplying a load of 10 W . Calculate the duty ratio, D .
13. A dc-dc converter has diode voltage and current as shown in the figure given below. The source voltage, $V_s = 12\text{ V}$, duty ratio, $D = 0.6$, switching frequency, $f_s = 25\text{ kHz}$, inductance, $L = 250\text{ }\mu\text{H}$ and filter capacitance is $C = 220\text{ }\mu\text{F}$. For average load current, $I_a = 1.5\text{ A}$, determine:
- average output voltage, V_a
 - peak-to-peak output ripple voltage, ΔV_C
 - peak-to-peak ripple current of inductor, ΔI_L
 - critical values of L and C

