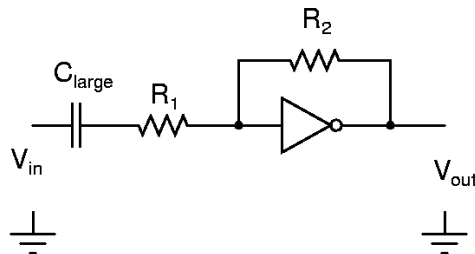


Experiment 2: Amplifier compensation

- 1) If $R_1 = 5k\Omega$ in all the experiments, what is the constraint on C_{large} ?
- 2) If you use a polarized capacitor for C_{large} , which side should be the positive terminal? You have to decide this based on the total voltage across the capacitor.
- 3) What is the expected total voltage at the junction of R_1 and R_2 assuming that the amplifiers are stable?
- 4) What is the transfer function of the circuit below? Model the inverter as a voltage controlled current source of value g_m and assume that C_{large} is infinite.



- 5) What is the transfer function of the circuit below? What is the dc gain? Model the inverters as voltage controlled current sources of value g_m and assume that C_{large} is infinite. Also find the transfer function when $R_c=0$. (Think about what difference you would see in the step response experiments between these two cases)

