

Experiment 1: Inverter characteristics

- 1) In the first part where you determine the characteristics of the inverter as a transconductor, you will need to choose R_F and the opamp supplies correctly.
 - a) From the data sheet, find out the output swing limits of the opamp LM324 when $\{V_{cc}, V_{ee}\} = \{6V, 0\}$. The datasheet numbers maybe for different supplies, but assume that the overhead on the higher and lower sides are the same as what is given there.
 - b) If you have to measure up to $\pm 2mA$ while keeping the opamp within the swing limits, what is the constraint on R_F ? (In the experiment, you should choose R_F and the opamp supplies so that this measurement can be made properly)
- 2) What is the typical propagation delay of the inverter at a 6V supply? If this value is not given, interpolate between the given values.
- 3) In the last part, what is the constraint on C_{large} if the resistance to the right side of it is 250Ω and you use a 10kHz sinusoid?
- 4) If you use a polarized capacitor for C_{large} , which side should be the positive terminal? You have to decide this based on the total voltage across the capacitor.