

# VLSI group, IIT Madras

 Search


- [Home](#)
- [People](#)
- [Research](#)
- [Publications](#)
- [Teaching](#)
- [Prospective Students](#)
- [SMDP](#)
- [TI RAships](#)

## VLSI group, IIT Madras


### Double balanced mixer
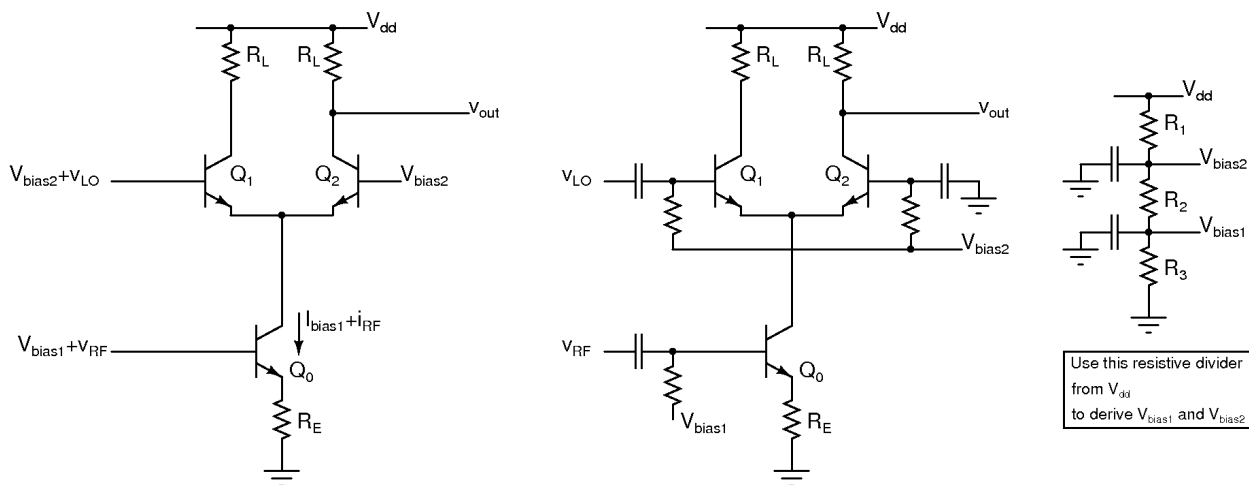
#### Goals


- Understand the operation of a double balanced mixer



- The above figure shows the mixer designed in the previous experiment. Ideally a mixer fed with  $V_{RF}$  and  $V_{LO}$  should have only product of these two components at the output. i.e the output should be zero if either of  $V_{RF}$  or  $V_{LO}$  is zero. But, as seen earlier, with  $V_{RF}=0$ , the above mixer still generates an output proportional to  $V_{LO}$  (LO feedthrough). Such a mixer is known as a single balanced mixer.
- LO feedthrough can be eliminated as shown in the circuit below by having two mixers driven by  $+V_{RF}$  and  $-V_{RF}$  and taking the difference between them. It can be seen by inspection that, when  $V_{RF}=0$ , the sum of currents through  $Q_1$  and  $Q_{2a}$  is a constant as is the sum of currents through  $Q_2$  and  $Q_{1a}$ . This is a double balanced mixer.

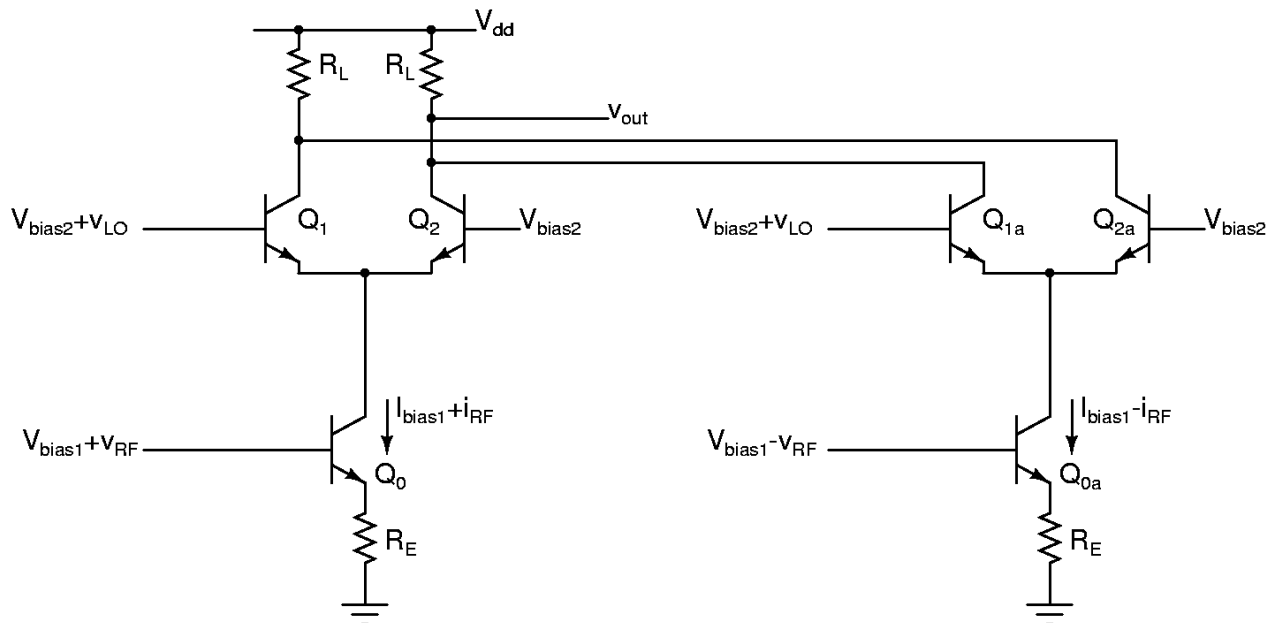

- The above circuit is available in the form of an IC-the MC1496 double balanced modulator. Its internal schematic is shown below. Most of the circuitry including the biasing arrangements are inside the IC. Only  $R_E$ , the load resistors, and the bias current setting resistor need to be connected externally. Compared to the circuit above, the bottom two transistors and their degenerating resistors are arranged as a differential pair inside the MC1496 integrated circuit.

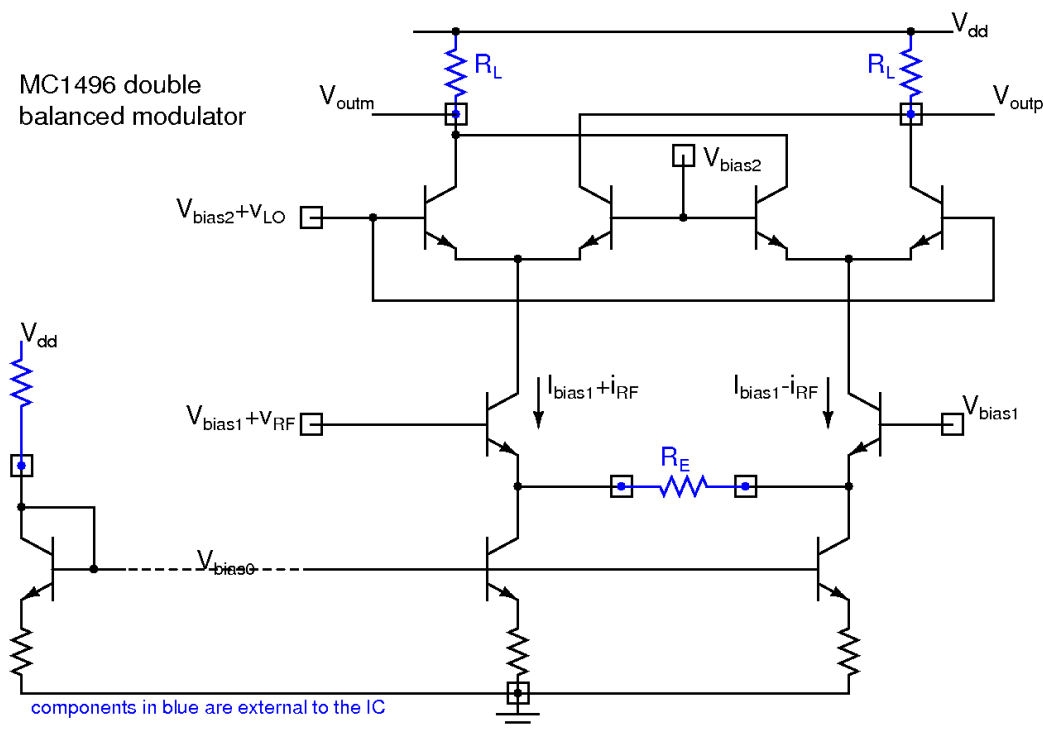

Use resistive dividers from  $V_{dd}$  to derive  $V_{bias1}$  and  $V_{bias2}$   
 Bypass the bias nodes  
 Use coupling capacitors as in the single balanced modulator  
 to drive  $v_{LO}$  and  $v_{RF}$

## To be done before the lab session

- Go through the lecture on double balanced mixers


[<http://www.ee.iitm.ac.in/~nagendra/EC330/200901/lectures/ec330-mixer2/ec330-mixer2.swf>].

- Design a double balanced mixer around the MC1496 IC. Use a 12V supply and 1mA current through the bias branch. The mixer should be able to take in an RF input peak of 1V and have a conversion gain(ratio of the *sinusoidal component* at  $f_{RF}+f_{LO}$  OR  $f_{RF}-f_{LO}$  at the differential output to the amplitude of the *input sinusoid*) of 4.
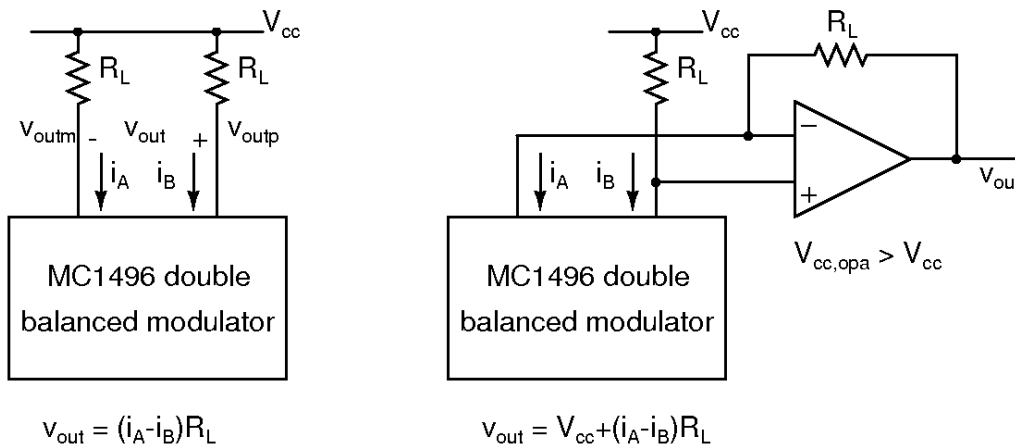
## To be done in the lab session

Verify the circuit designed above:

- Take  $V_{outp}$  or  $V_{outm}$  as the output.
- Drive the input with a low frequency  $v_{RF}$ (~ 1kHz) and a high frequency  $v_{LO}$ (~10kHz) and observe the output. You can use the oscillator designed in the previous experiment as the 10kHz source.
- Verify that the outputs are as expected.



- Build the differential to single ended converter shown above and drive it from the mixer. Choose appropriate supply voltages for the opamp.
  - Drive the mixer with a low frequency  $v_{RF}$  and a high frequency  $v_{LO}$  and observe the output.
  - Drive the mixer with a  $v_{RF}$  and  $v_{LO}$  at close by, but not identical frequencies and observe the low frequency( $f_{RF}-f_{LO}$ ) output. For filtering out the high frequency component, use a capacitor of appropriate value across  $R_L$ (both of them) which will short it out at high frequencies. Filtering will be a lot easier if you choose a higher  $f_{LO}$ , say 25kHz or 50kHz, and a difference frequency around 1kHz.
  - Remove the RF input and observe the output.
  - Remove the LO input and observe the output.

## Applications

- This circuit is very commonly used for frequency translation in radio transmitters and receivers.

## Something to try on your own

- Drive the lower input with audio, say from your computer or digital player. Drive the LO input with a sinusoid in the AM band(0.5-1.5MHz). You should be able to use an AM radio placed close by to receive the transmitted audio. You can use a short wire connected to the output node as an antenna.