

~~MyCopy~~ MyCopy

$$kx < 0 \\ \Rightarrow R_1 < R_2$$


To find out sign of kx , check V_c at $t = T_1$.

If $V_c > 0 \Rightarrow kx > 0$

$V_c = 0 \Rightarrow kx < 0$

LOAD CELL

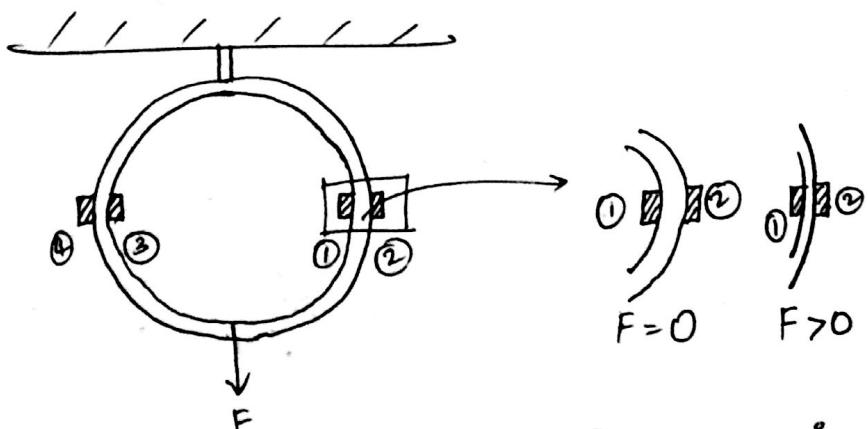- Usage of strain gauge to measure force.
- Proving ring:




① : expansion
② : contraction

①, ③ : $R \uparrow \text{ces}$

②, ④ : $R \downarrow \text{ces}$

- Can be used until $F \approx 50 \text{ kg}$.

- What about $F > 50 \text{ kg}$?

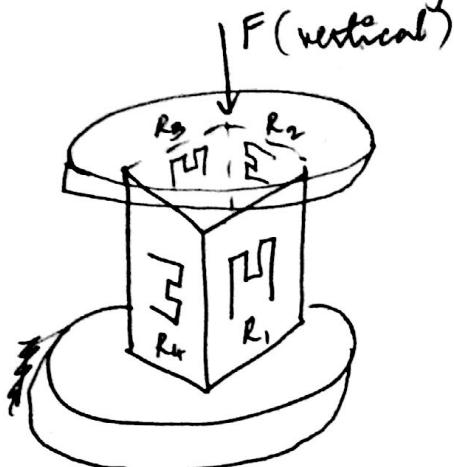


$$R_1 \quad R_2 \quad R_3 \quad R_4$$

| | | | |
|------------|-------------------|------------|-------------------|
| \uparrow | \leftrightarrow | \uparrow | \leftrightarrow |
|------------|-------------------|------------|-------------------|

↔ : sensitivity axes


Using poison ratio, we can use R_1, R_2, R_3, R_4 in a full bridge

If F is at an angle:

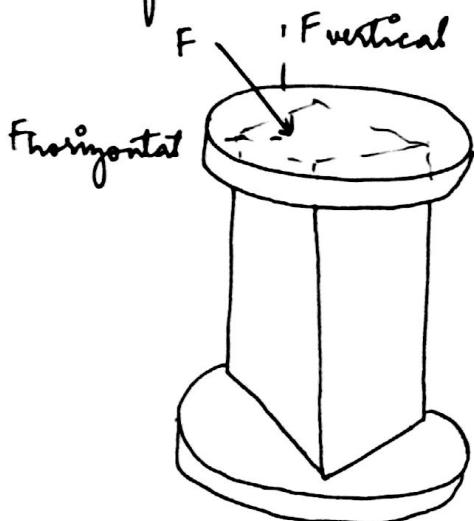



There will be strain due to horizontal comp. of F .
But, we want to see only
• influence of vertical comp.
(ie; it must not be sensitive to bending/
shear force).

So, then use 8 sided polygon:

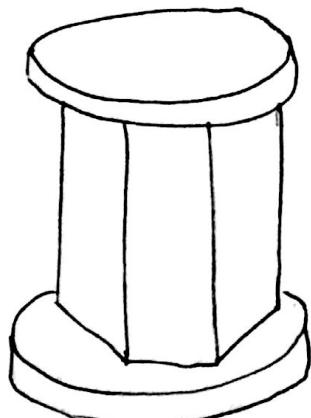

| | | | | | | | |
|------------|-------------------|------------|-------------------|------------|-------------------|------------|-------------------|
| \uparrow | \leftrightarrow | \uparrow | \leftrightarrow | \uparrow | \leftrightarrow | \uparrow | \leftrightarrow |
|------------|-------------------|------------|-------------------|------------|-------------------|------------|-------------------|

Cross section:

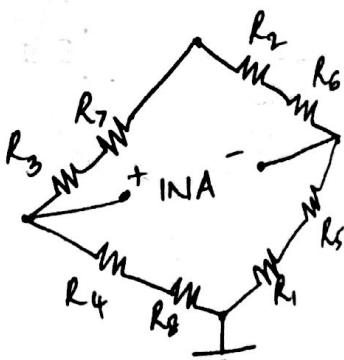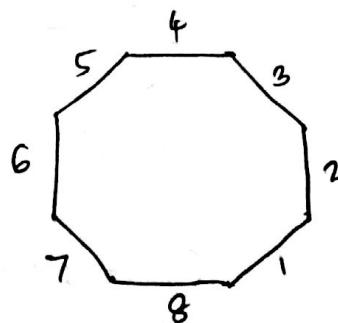

Now, 5 elongates as much as 1 contracts
net shear force


Similarly, 4, 8; 6, 2; 7, 3;

So, use these pairs in each arm of bridge.

MyCopy


Torque

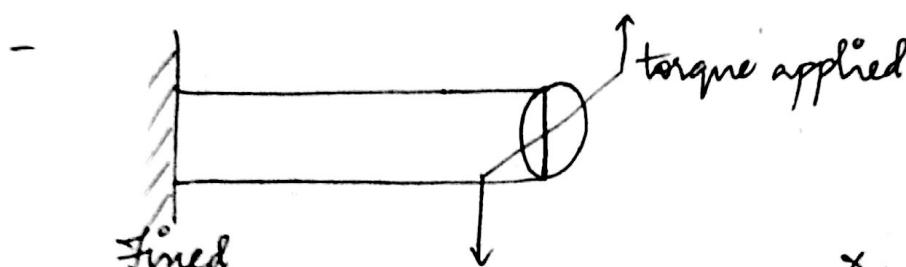- $\tau = \text{Force} \times \text{Distance}$




Finally aligns to 45° axis.

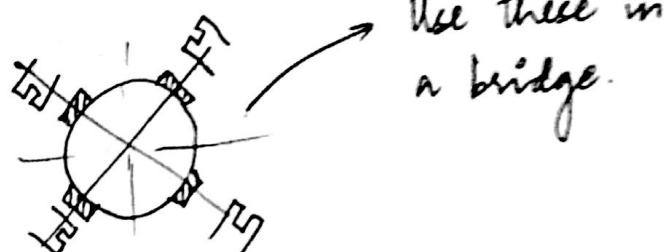So, put strain strain gauges
at $45^\circ, 135^\circ, -45^\circ, -135^\circ$.




If we can't have electrical connections to these gauges because of twisting, what do we do?

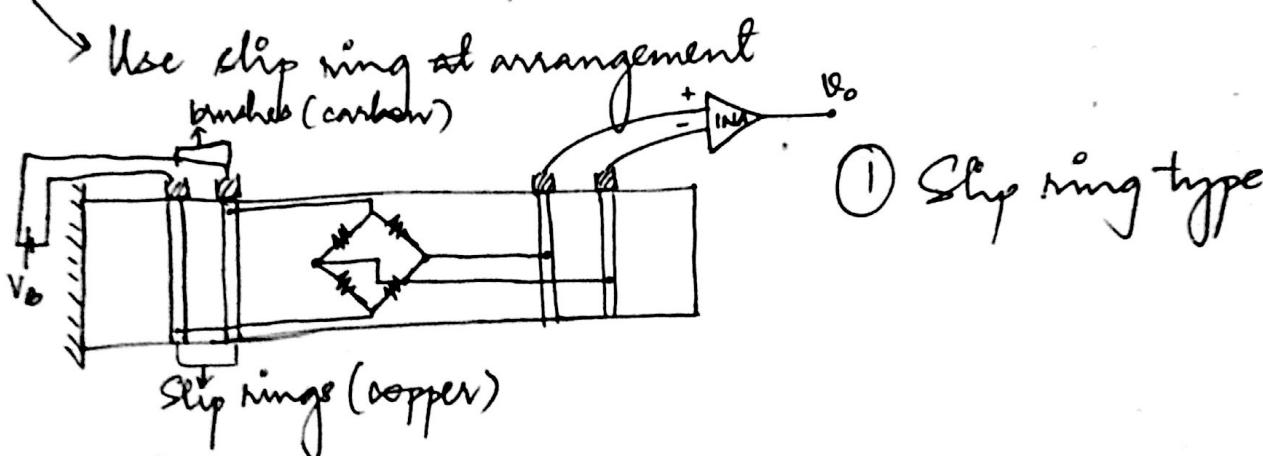A differential element after twisting becomes elongated along 2 directions resp.




① Slip ring type

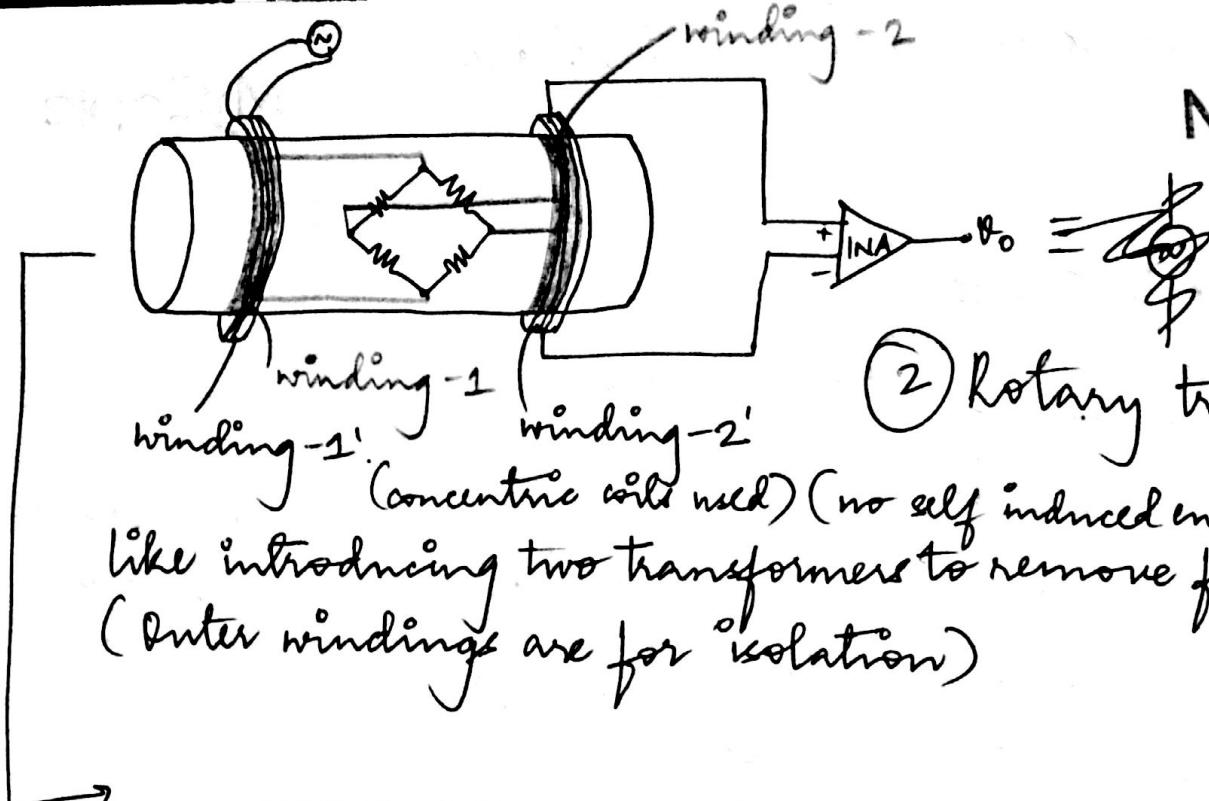
Issue is that there is friction at electrical contacts b/w rings & brushes which are subjected to wear. This could introduce some loading on the rotation.



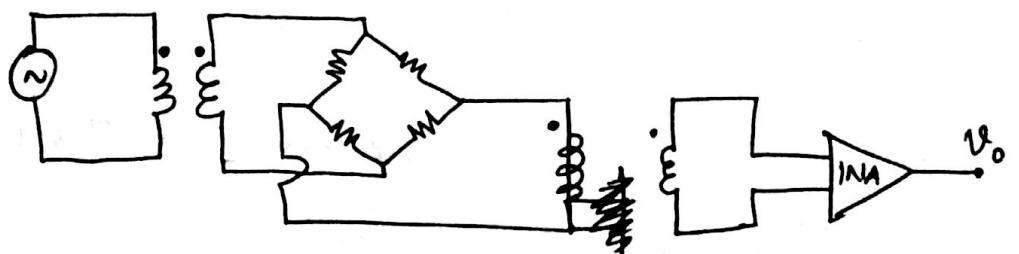② **Rotary transformer**
 (concentric coils used) (no self induced emf)
 like introducing two transformers to remove friction & wear
 (Outer windings are for "isolation")





③ Telemeter: To reduce size

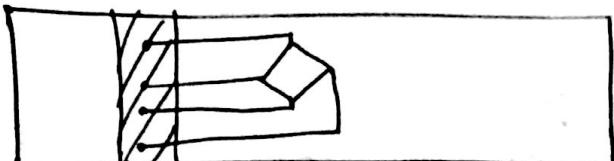

MU

MU: Measurement Unit
 (some electronics)

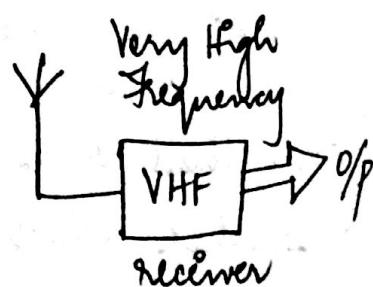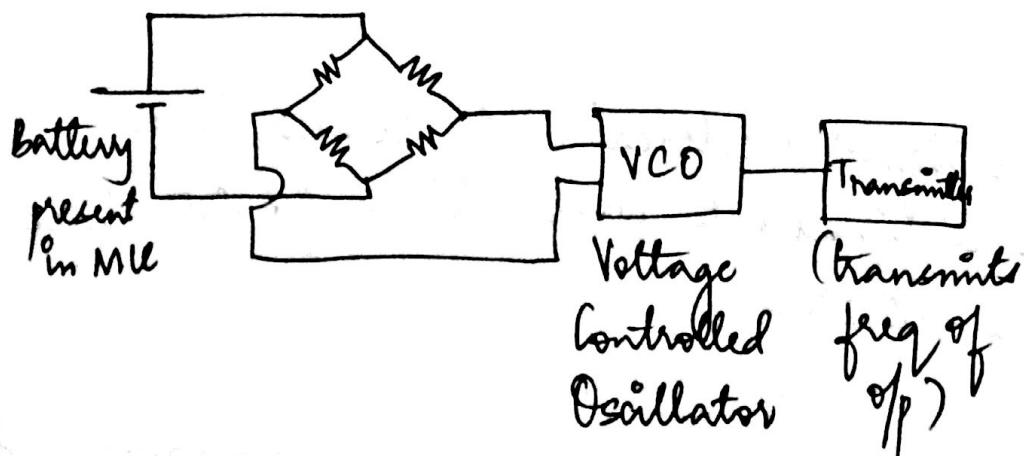

Characteristics of sensors

MyCopie


1. Range : For i/p & o/p
2. Accuracy
3. Sensitivity = $\frac{\Delta \text{O/P}}{\Delta \text{i/P}}$ (Gauge factor = $\frac{\Delta R/R}{\Delta \text{I/P}}$) ; more sensitive \rightarrow 1 per cent
4. Linearity : Non-linearity = Largest deviation from linearity
5. Threshold : Min. i/p to have non-zero o/p
6. Resolution : Smallest quantity that can be measured.
7. Dead-band ; 8. Precision :

Sensors have steady state and dynamic performance.

Eg:- Proving ring:

i/p : $0 - 50 \text{ Kg} \equiv 50 \text{ Kg range}$ if range is always $[0, \text{Range}]$
 o/p : $-5V - 5V \equiv 10V \text{ range}$


- Dead band :

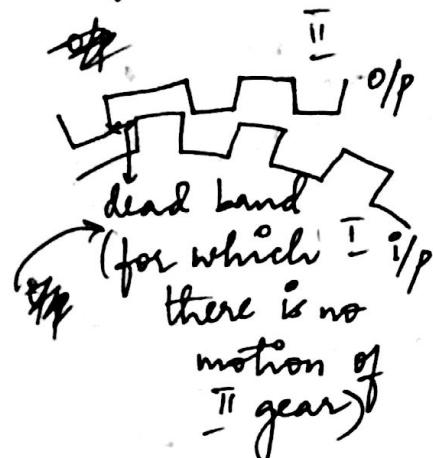

Order of system = No. of ^{distinct} storage elements




Lab experiment 4

Rectifier circuit is not ideal

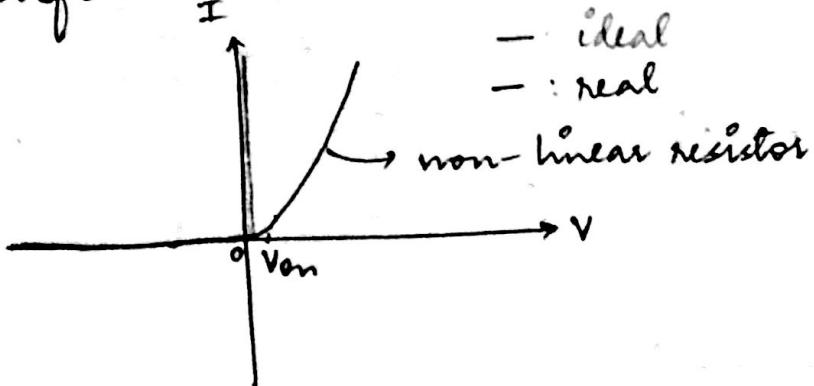

Precision rectifier - Diode which is made ideal using additional electronics.

MyCopy

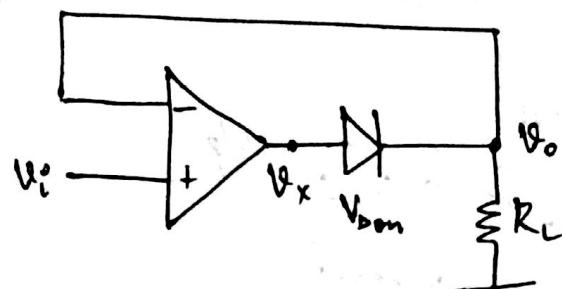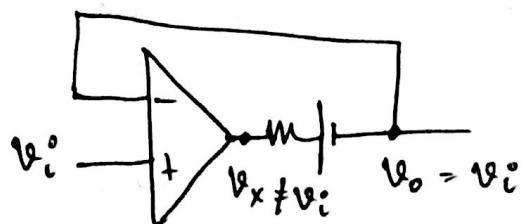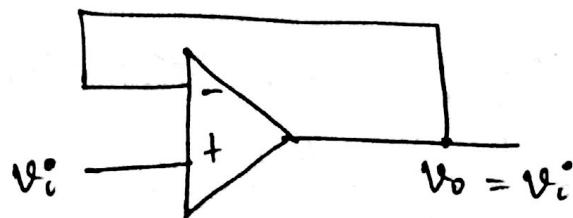


Suppose diode is off, $V_o = 0$ [$\because i_- = 0$]

$$\Rightarrow V_x = V_{sat}$$

\Rightarrow Diode turns on.

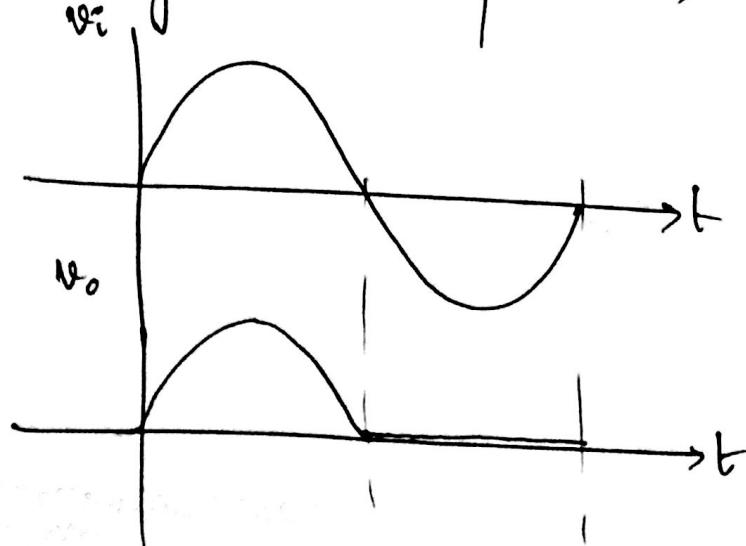As long as V_i is positive, diode is on and $V_o = V_i$.



So, non-idealities
of diode are
removed
 \rightarrow Super diode

$V_i < 0$: Diode off $\Rightarrow V_x = -V_{sat}$

Diode off

$$\Rightarrow V_o = 0$$

My Copie

$$\text{Slew rate!} = \frac{dV_o}{dt}$$


But, in the next +ve cycle, V_x must go from $-V_{sat}$ to 0

In LF34L, slew rate = $13V/\mu s$

If $V_{sat} = 13V$, we require $1\mu s$ for V_x to come back to 0


For $V_i \sim \frac{1}{2}\text{MHz}$, you lose like $\frac{1}{2}$ a cycle!

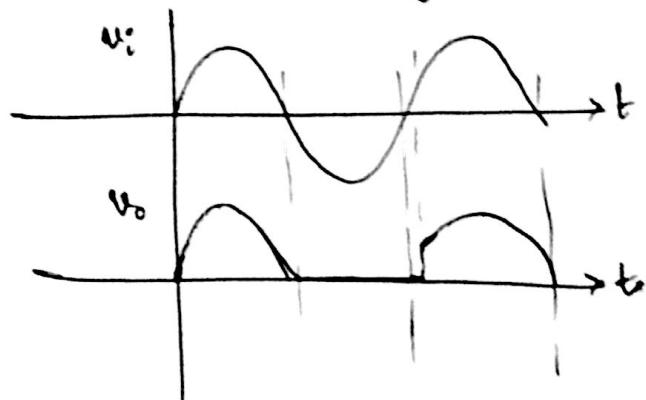$V_i \sim 1\text{Hz}$, you lose \sim a few μs \rightarrow Not an issue!



Opamp has many poles \rightarrow Dominant pole / frequency compensation

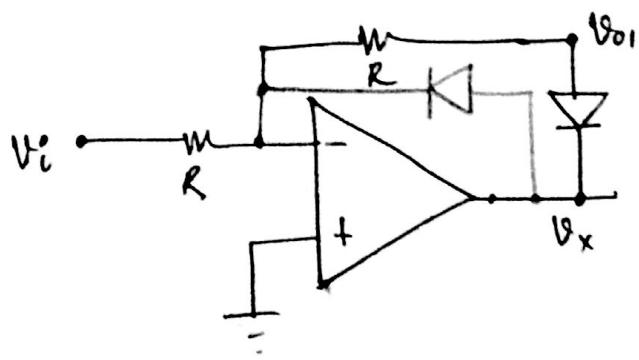Slew rate determined by capacitor used above.



$V_i > 0$ (assume diode off)

$$\Rightarrow V_x = -V_{sat}$$

Diode on \nwarrow Feedback on!

$V_i < 0$: Issue!

Introduce $-V_{dd}$ so that swing

"Don't Think Just Do It"




is b/w $-V_{dd}$ to $+V_{dd}$ \rightarrow b/w

slew rate reqd



Can use at higher frequencies!

But, this is still only a $\frac{1}{2}$ wave rectifier! MyCopy

Above gives:

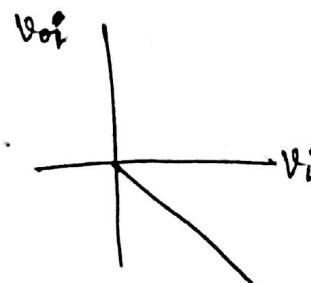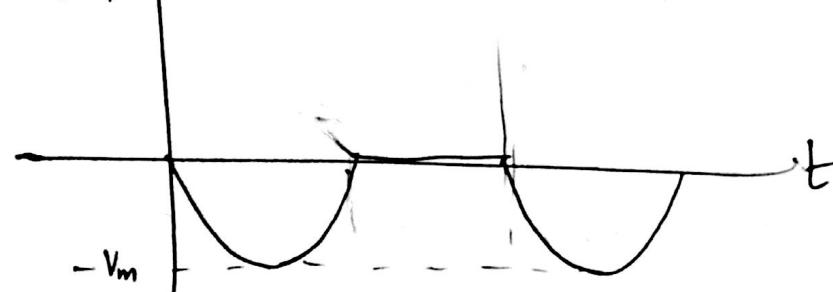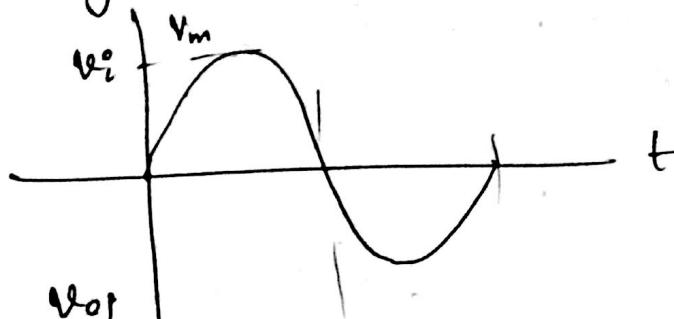


If we want

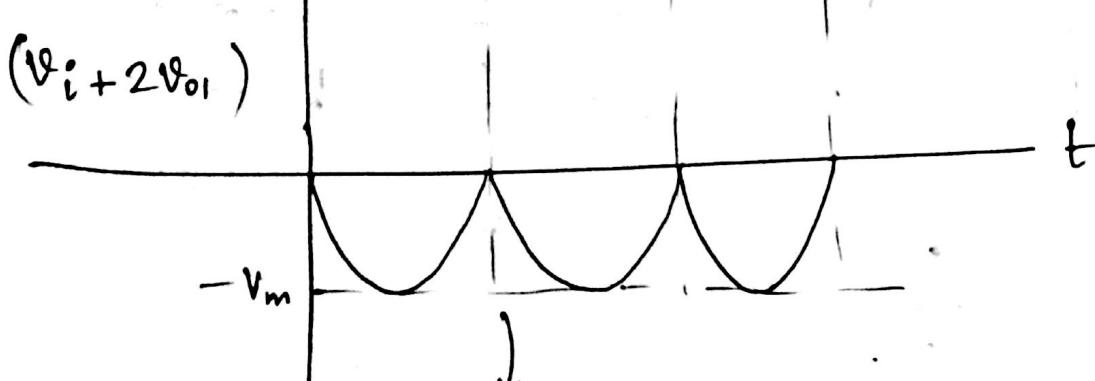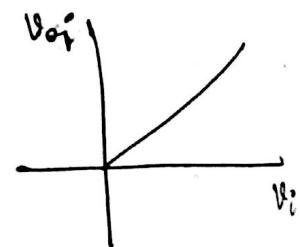

This needs to be inverted.


Use an "inverting summing amplifier"

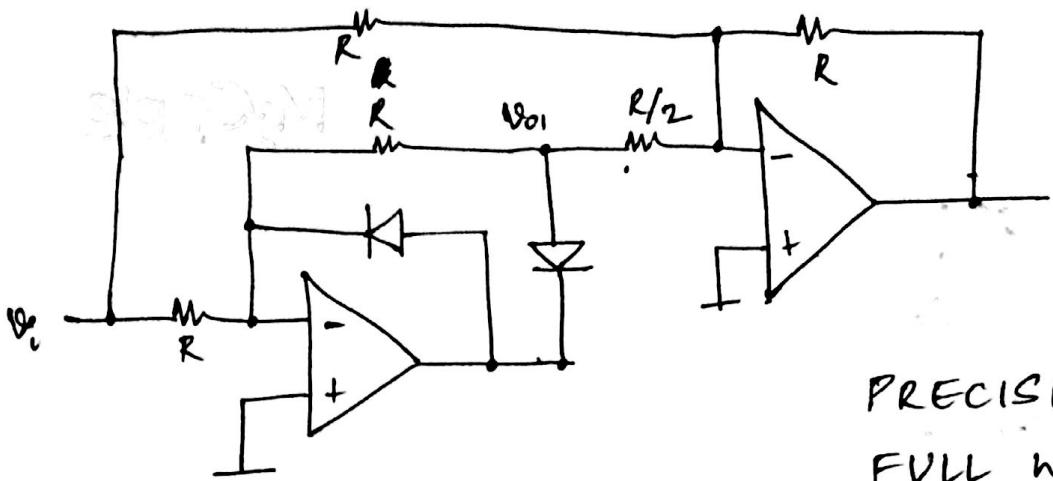

MyCopie

PRECISION FULL WAVE RECTIFIER

but, meter has resistance.

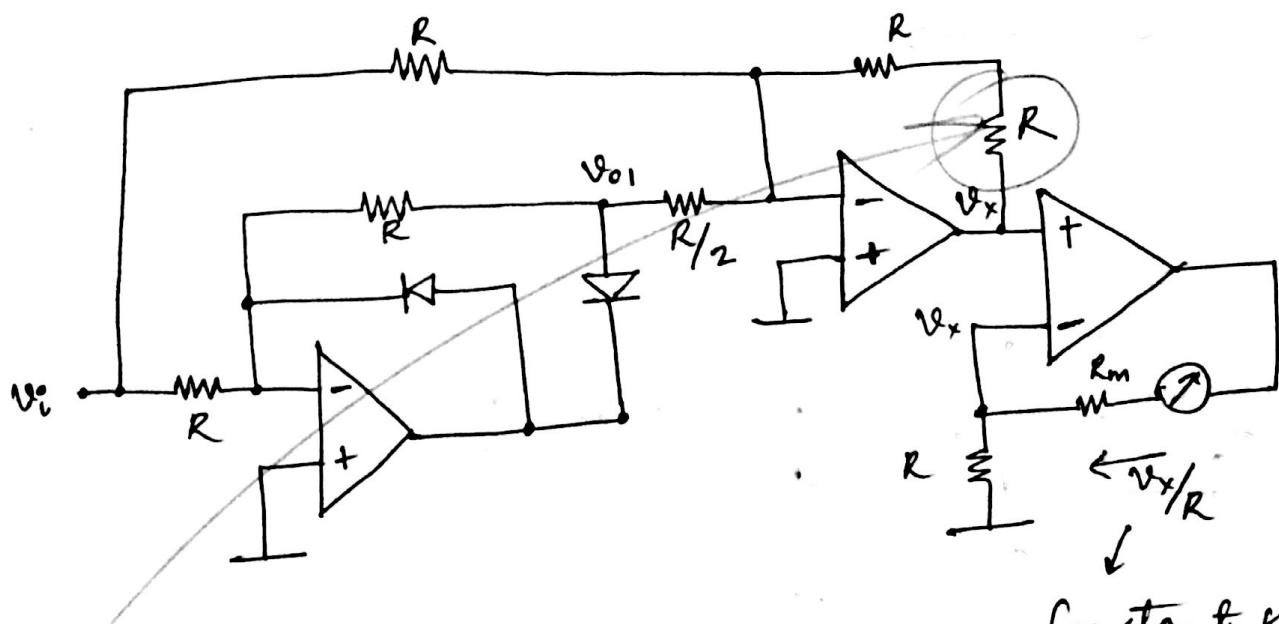

Constant current
irrespective of variation
in R_m



$$0 - 5V \Rightarrow 5V \text{ RMS}$$

Find V_x avg value.


$$V_{avg} = 5\sqrt{2} \times \frac{2}{\pi}$$

$$I_{full\ scale} = \frac{1}{R} \times \frac{10\sqrt{2}}{\pi}$$


My

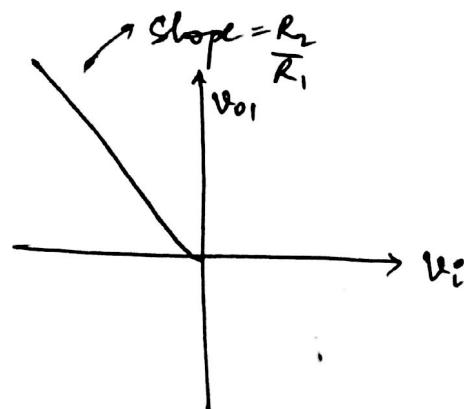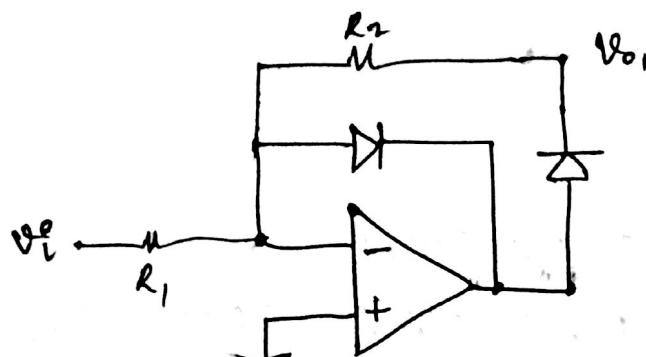

25/2/16

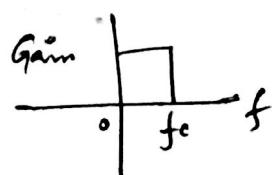

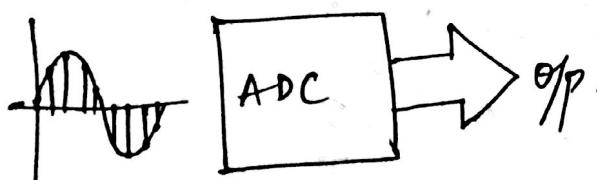We can do this in analog digital domain too :




Sampling
rate must
be sufficient
to sample the
i/p sinusoid
Sampling > f_s

"Don't Think Just Do"
— My

If digitization is done after filtering,

MyCopic
Digitizing the world

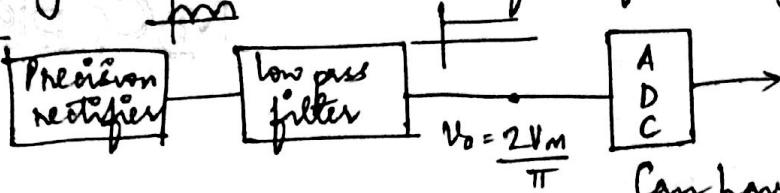

Can have

low sampling rate
since nearly constant
signal is the ipf.

Noise and Interference

Noise: Inherent from a device.

Interference: Unwanted signals coming from external sources.

- Thermal noise (in resistors, ...) : Random motion of e⁻s/ holes

$$\text{Thermal noise power } Et^2 = 4kTR_B$$

↓ resistance ↓ bandwidth

- Shot noise : Charge carriers crossing potential barrier.

- Flicker noise : Charge traveling semiconductor encounters traps.

Due to noise, resolution gets affected.


Eg:- Temp. sensor : $10\mu V/\text{°C}$

Resolution : $1\mu V$

⇒ Can measure 0.1°C .

If noise : $2\mu V \Rightarrow$ resolution $\geq 0.2\text{°C}$. Anything less than 0.2°C , you can't resolve.

To measure a source V_s :

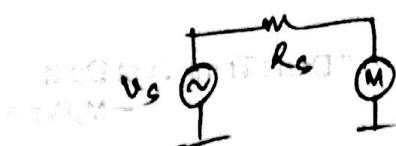


Can't be used since there is loading

"Don't think Just Do It"
— MyCopic


Use an opamp!

MyCopicie

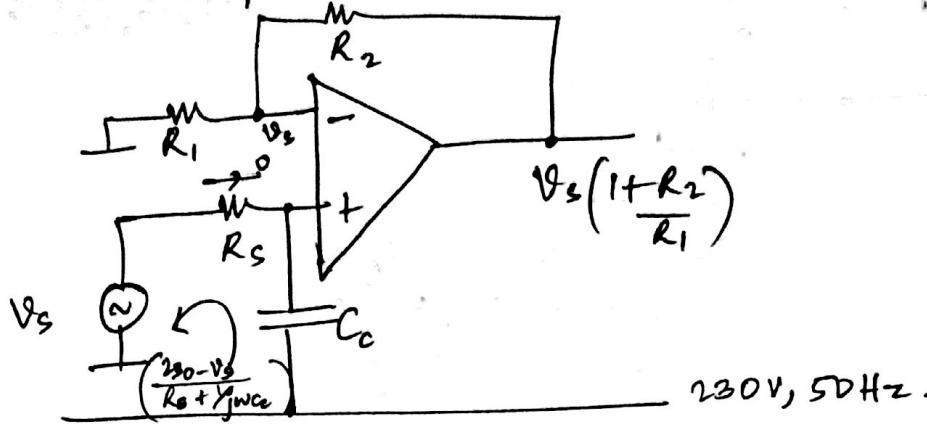


Suppose there is a 230V supply nearby. There is capacitive coupling \Rightarrow current drawn.

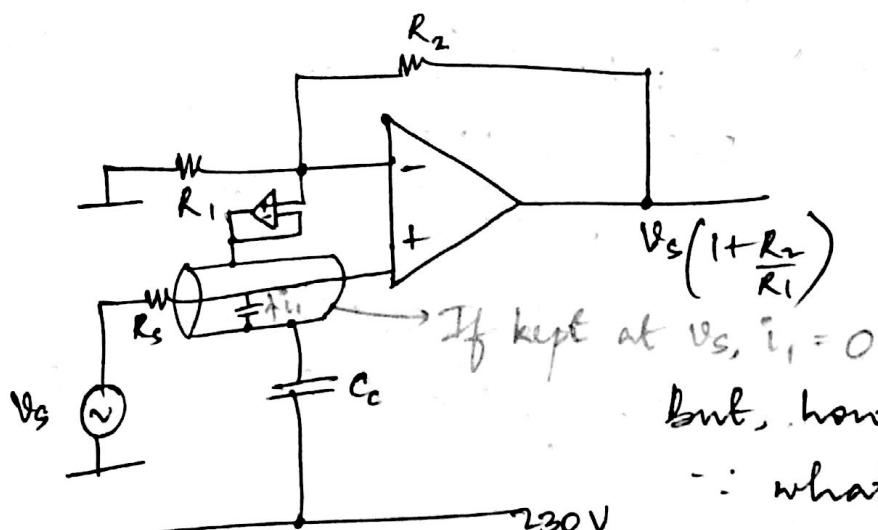
Insert a metallic tool surrounding R_s wire.



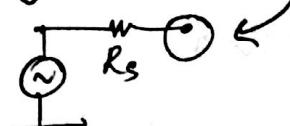But, how will you keep it at V_s ?
∴ what you have is



Use a buffer!

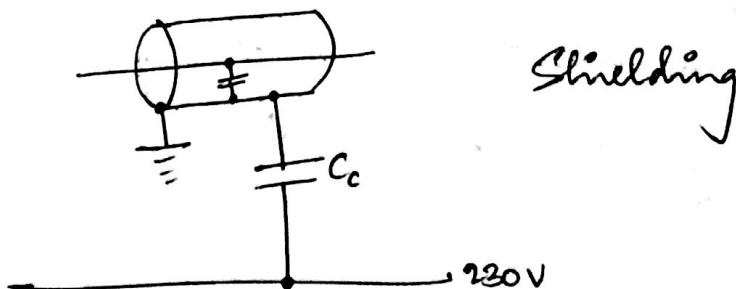

If buffer is used, power is used. It is driven. Called guardin
MyCopic

So far, bridge was excited by DC.

If you excite it at f_B , take its op only at f_B using a filter. \Rightarrow Interference doesn't come into picture.

If bridge is excited using $V_x = \sqrt{2} V_R \sin \omega t$, ($V_R = R_{MS}$)

At filter op, we get $V_x = \sqrt{2} V_R \sin(\omega t + \Theta)$


We are interested in V_x & Θ .

$$V_R - \xrightarrow{\text{X}} 2V_R V_x \sin(\omega t + \Theta) \sin \omega t$$

$$= V_R V_x [\cos(\Theta) - \cos(2\omega t + \Theta)]$$

$$\text{Avg value of this} = \frac{1}{T} \int_0^T V_R V_x (\cos \Theta - \cos(2\omega t + \Theta)) dt$$

$$V_{o1} = V_R V_x \cos \Theta$$

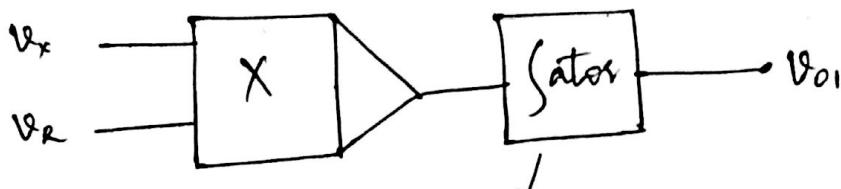

Can be realised
using a LPF

$$\text{If } V_R = \sqrt{2} V_R \sin(\omega t + 90^\circ),$$

$$V_{o2} = V_R V_x \sin \Theta$$

$$V_o = \sqrt{V_{o1}^2 + V_{o2}^2} = V_R V_x$$

$$\therefore V_x = \frac{V_o}{V_R}$$

$$\cos \Theta = \frac{V_{o1}}{V_R \cancel{V_x}} = \frac{V_{o1}}{V_o}$$


~~S~~
SYNCHRONOUS
DEMODULATION

(Even if there are
↑er harmonics in V_x ,
 V_{o1} = only DC component)

Last Class

- Noise & Interference
- Multiphase type Synchronous Demodulator
or

Multiphase type PSD
Phase Sensitive

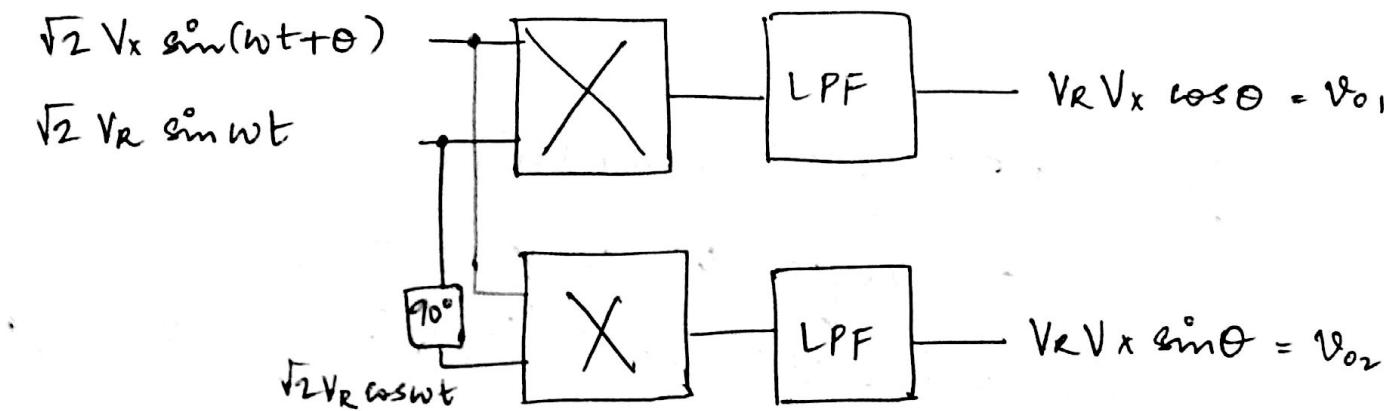

$$V_o = \sqrt{V_{o_1}^2 + V_{o_2}^2} = V_R V_x$$

We know $V_R \Rightarrow V_x = \frac{V_o}{V_R}$

$$\theta = \tan^{-1}\left(\frac{V_{o_2}}{V_{o_1}}\right)$$

LOCK-IN AMPLIFIER

(\therefore op locked to freq w ,
no other freq present)

This is useful as long as noise is at different frequency than signal (here, w).

If noise is @ w , we can't do much!


But, multipliers are expensive! Cheap ones are inaccurate!
Use something else apart from multipliers.

— Shielding
— Guarding


MyCopie

$\sqrt{2} V_x \sin(\omega t + \theta)$

MyCopic

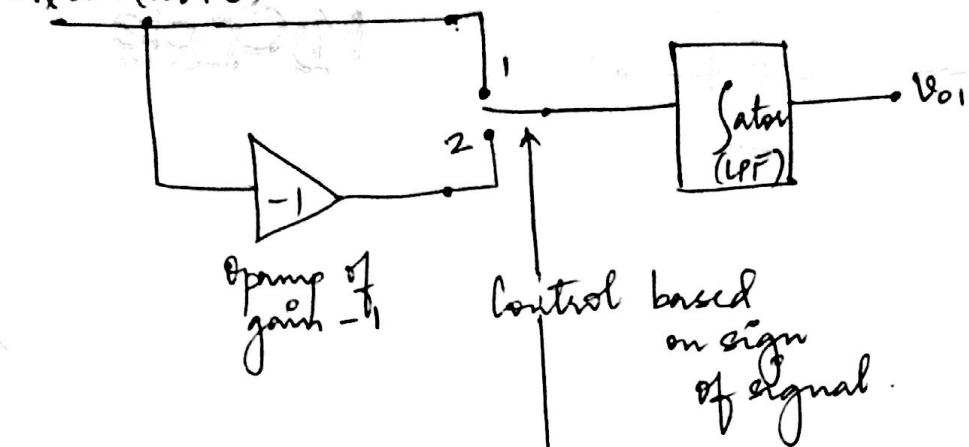

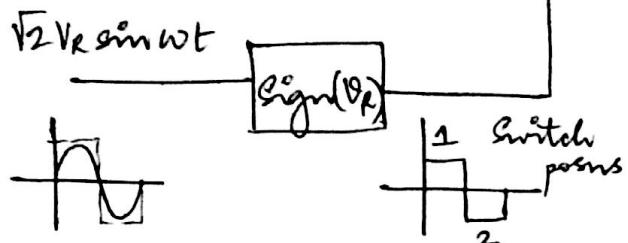SWITCHING TYPE
PSD or
SYNCHRONOUS
DEMODULATOR



$$V_{o1} = \frac{1}{T_0} \left(\int_0^{T_0/2} \sqrt{2} V_x \sin(\omega t + \theta) dt + - \int_{T_0/2}^{T_0} \sqrt{2} V_x \sin(\omega t + \theta) dt \right)$$


$$= \frac{\sqrt{2} V_x}{T_0} \left[\frac{T_0}{2\pi} \left(\cos(\theta) \cos(\theta + \pi) + \cos(\theta + 2\pi) - \cos(\theta + \pi) \right) \right]$$

$$= \frac{V_x}{\sqrt{2}\pi} \left(\cos \theta + 2 \cos \theta + \cos \theta \right)$$




$$\cancel{\frac{V_x}{\sqrt{2}\pi} (1 - \cos \theta)}$$

$$V_{o1} = \frac{2\sqrt{2} V_x}{\pi} \cos \theta$$

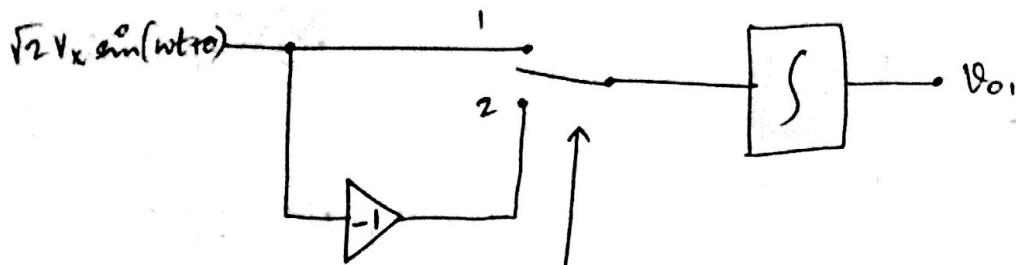Precision rectifier realizes the same for $\theta = 0$.



MyCopie

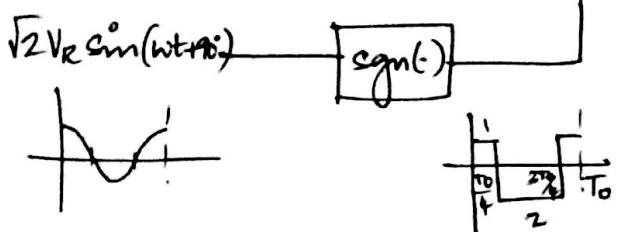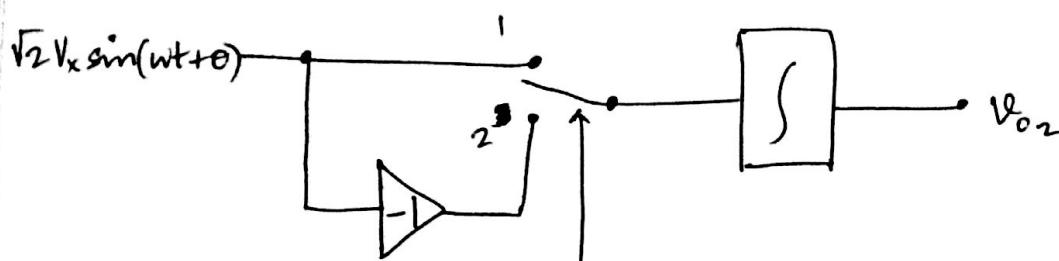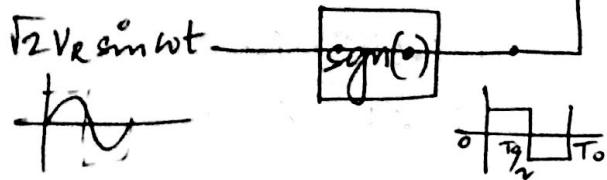

$$V_{o2} = \frac{1}{T_0} \left[\int_0^{T_0/4} \sqrt{2}V_x \sin(\omega t + \theta) dt - \int_{T_0/4}^{3T_0/4} \sqrt{2}V_x \sin(\omega t + \theta) dt + \int_{3T_0/4}^{T_0} \sqrt{2}V_x \sin(\omega t + \theta) dt \right]$$

$$= \sqrt{2}V_x \cdot \frac{T_0}{2\pi} \left[\cos\theta + \sin\theta + \sin\theta + \sin\theta + \sin\theta - \cos\theta \right]$$

$$V_{o2} = \frac{2\sqrt{2}V_x \sin\theta}{\pi}$$

$$V_{o1} = \frac{2\sqrt{2}V_x \cos\theta}{\pi}$$

$$V_o = \sqrt{V_{o1}^2 + V_{o2}^2} = \frac{2\sqrt{2}V_x}{\pi}$$


$$V_x = \frac{\pi V_o}{2\sqrt{2}}$$

$$\theta = \tan^{-1} \left(\frac{V_{o2}}{V_{o1}} \right)$$

Issues!


MyCopic

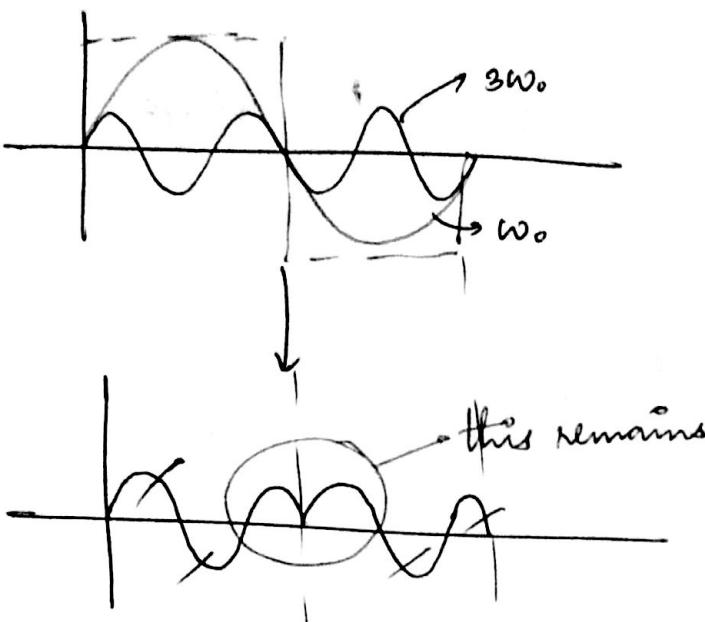- Switch can have delay
- ADG30 - switching type PSD.
- If ~~this~~ V_x has other harmonics:





So, odd harmonics don't give o/p.

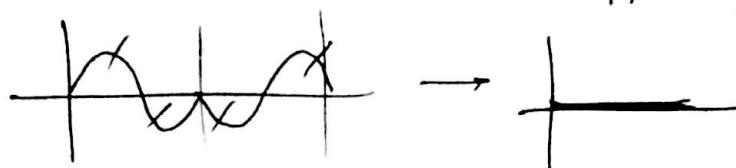Even harmonics have ~~not~~ 0 o/p as ~~they~~



Lab:

- ① Realise LPF

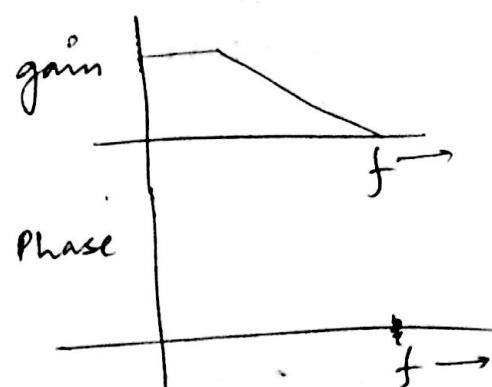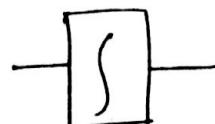

- II order LPF \Rightarrow Apply step input, find tsettling

"Don't Think Just Do It"

— MyCopic


Interference

MyCopicie

- ① Conductive coupling
- ② Capacitive coupling
- ③ Magnetic coupling


Though we can obtain clean op from noisy signal using PSD, we require ways to reducing interference cause this noise could saturate opamps! (?::)

① Conductive coupling:

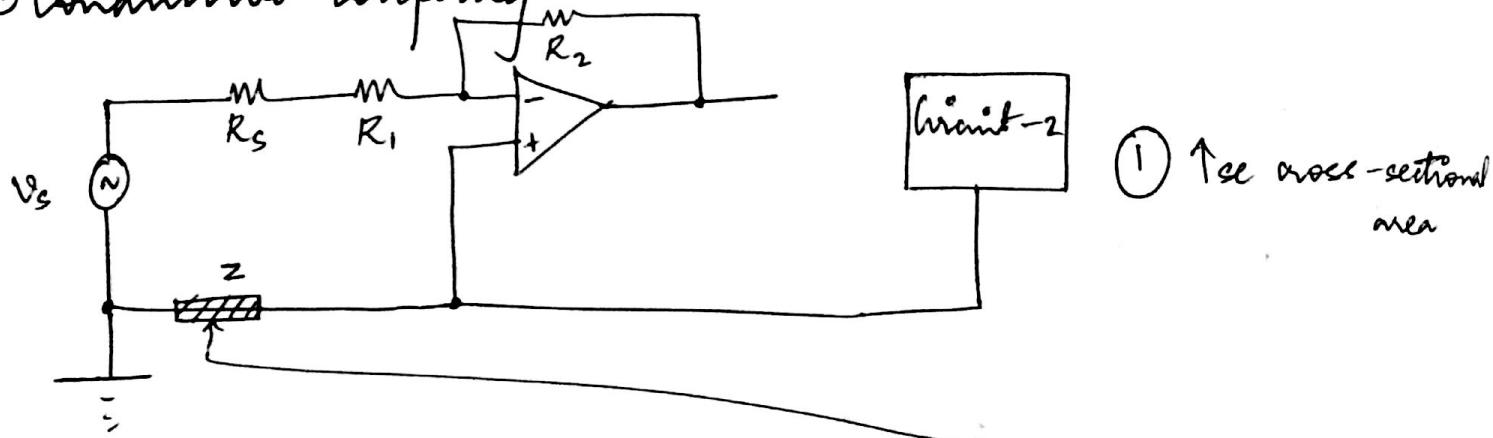

Supposing your wire has impedance z . Then, there is voltage drop across it depending on frequency of operation. This gives wrong op at opamp op.

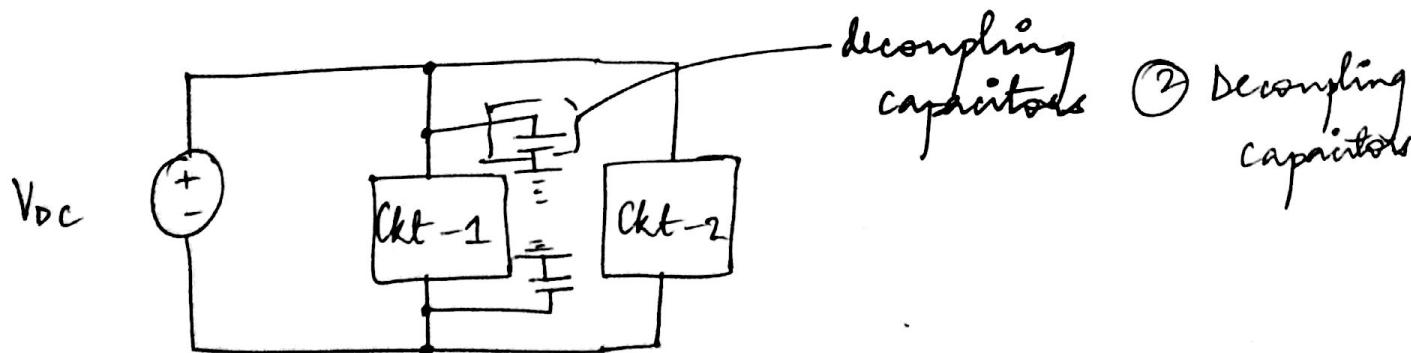So, reduce z by ↑ing cross-sectional area of ground track.




Add capacitors so as to be able to give any high frequency current reqd by ckt & prevent this ↑ freq ckt from flowing back thro V_{oc} .

"Don't Think Just Do It"
—MyCopicie


Digital ckt's usually have lot of transients during switching due to switching. So, have separate grounds for analog & digital ckt's. ③ Separate ground for A, D

③ Magnetic coupling:

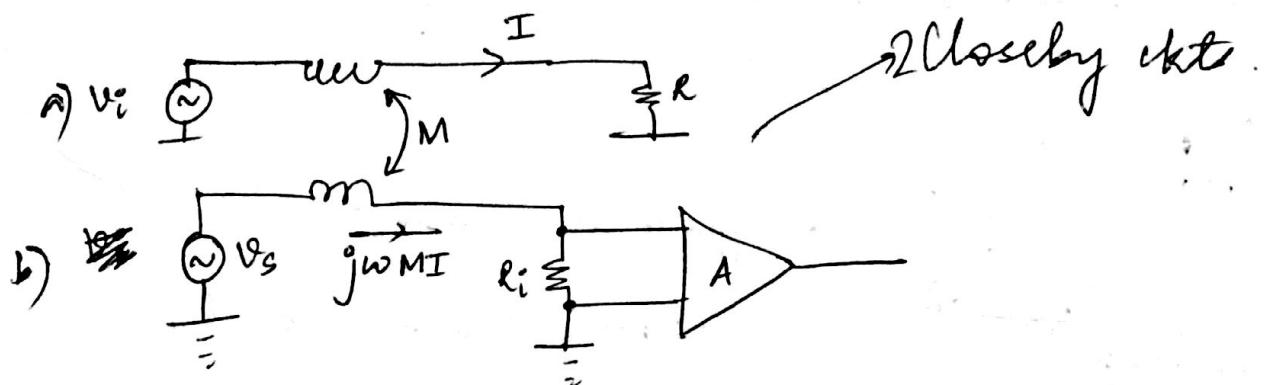



So, there will be o/p in b) due to current in a). due to magnetic coupling.

If they are arranged as

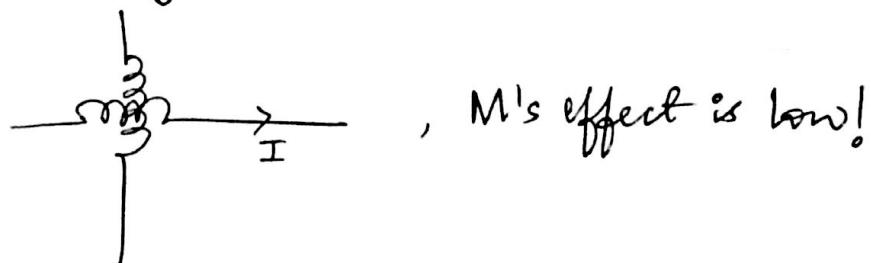


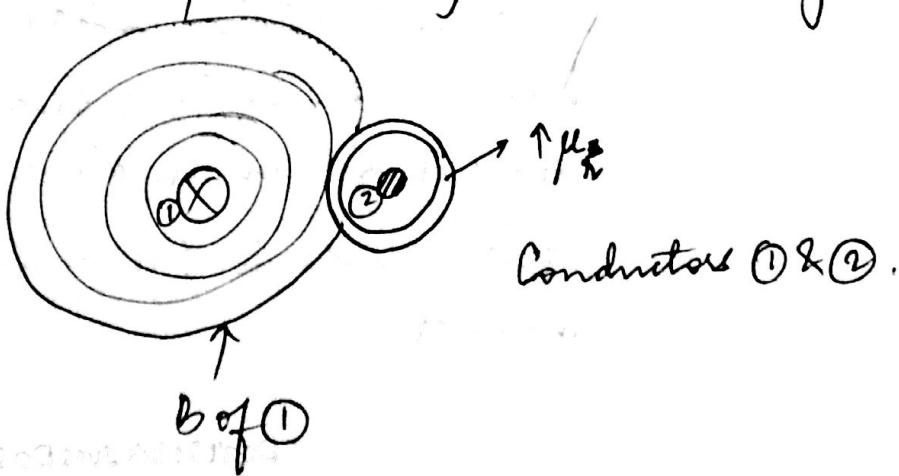
So, what you do is introduce a tube of low reluctance ↑ relative permeability ~~not~~ → Magnetic shielding.



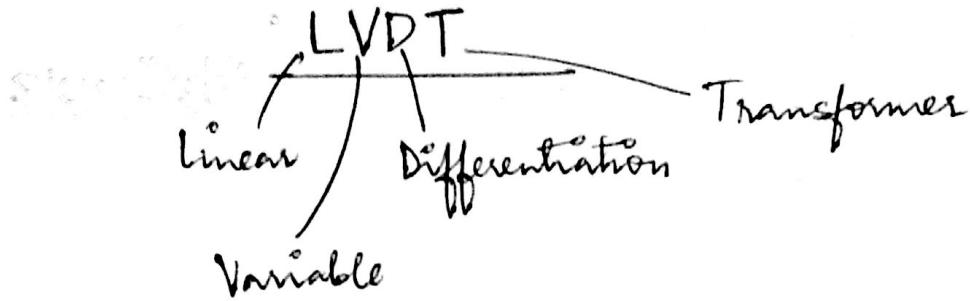


MyCopicie

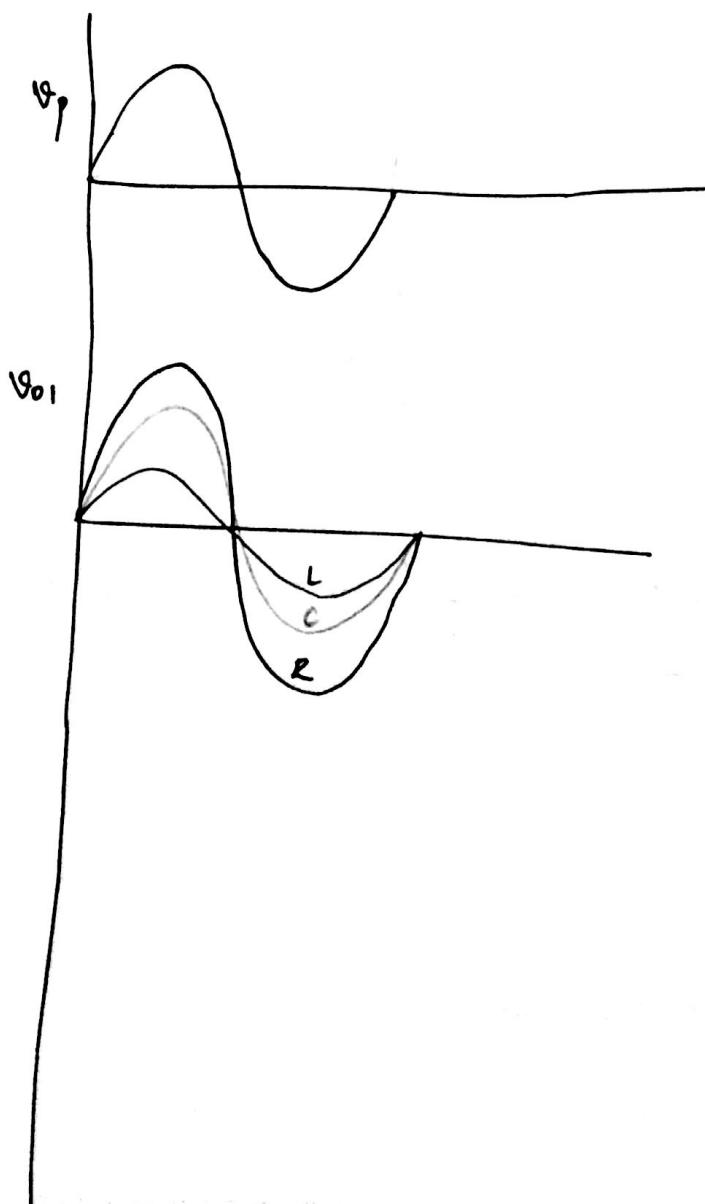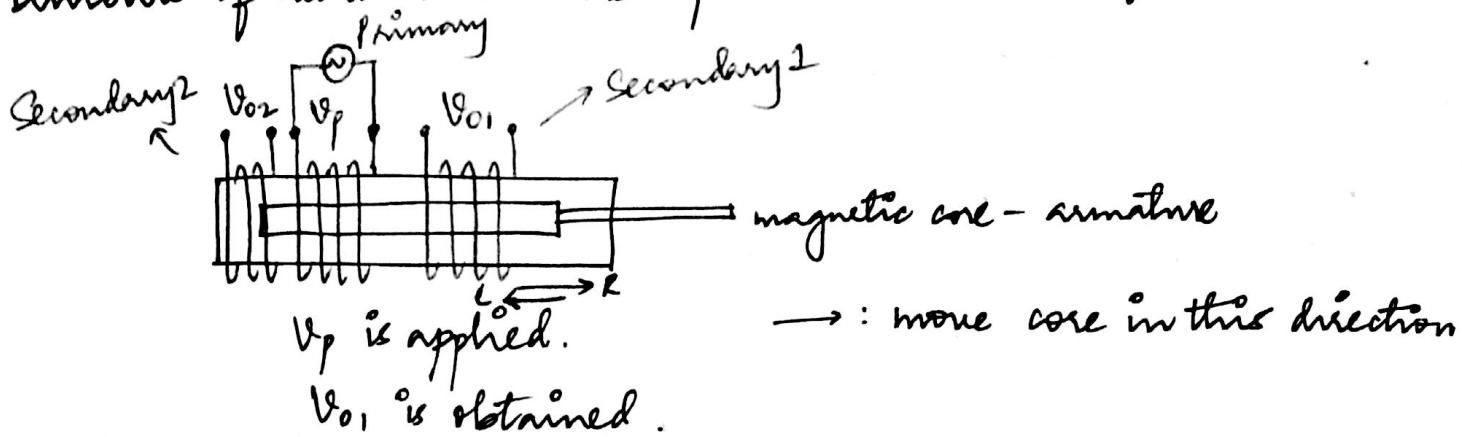Demerits of resistive sensors - power loss due to friction.







L: left
C: center
R: Right

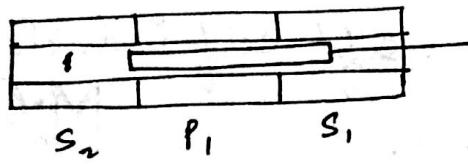We wish to obtain difference b/w L & R. So, introduce another coil on the other side which reads in the opposite manner.



MyC_opie

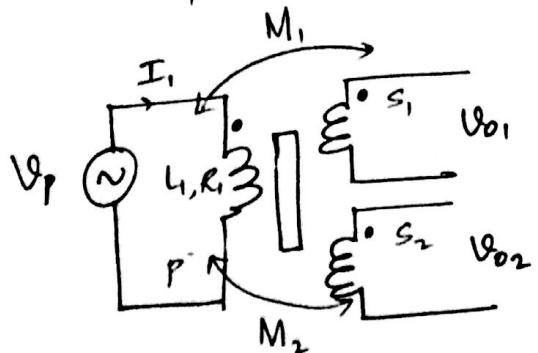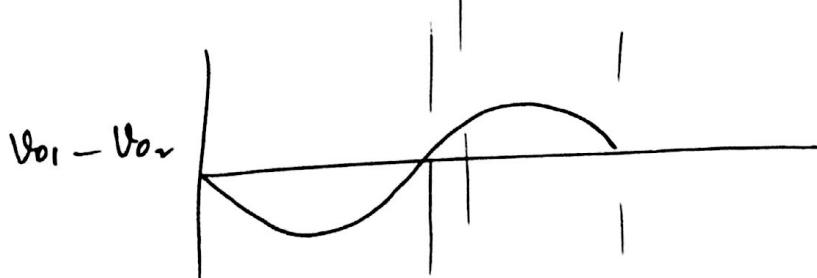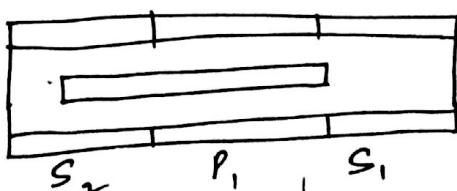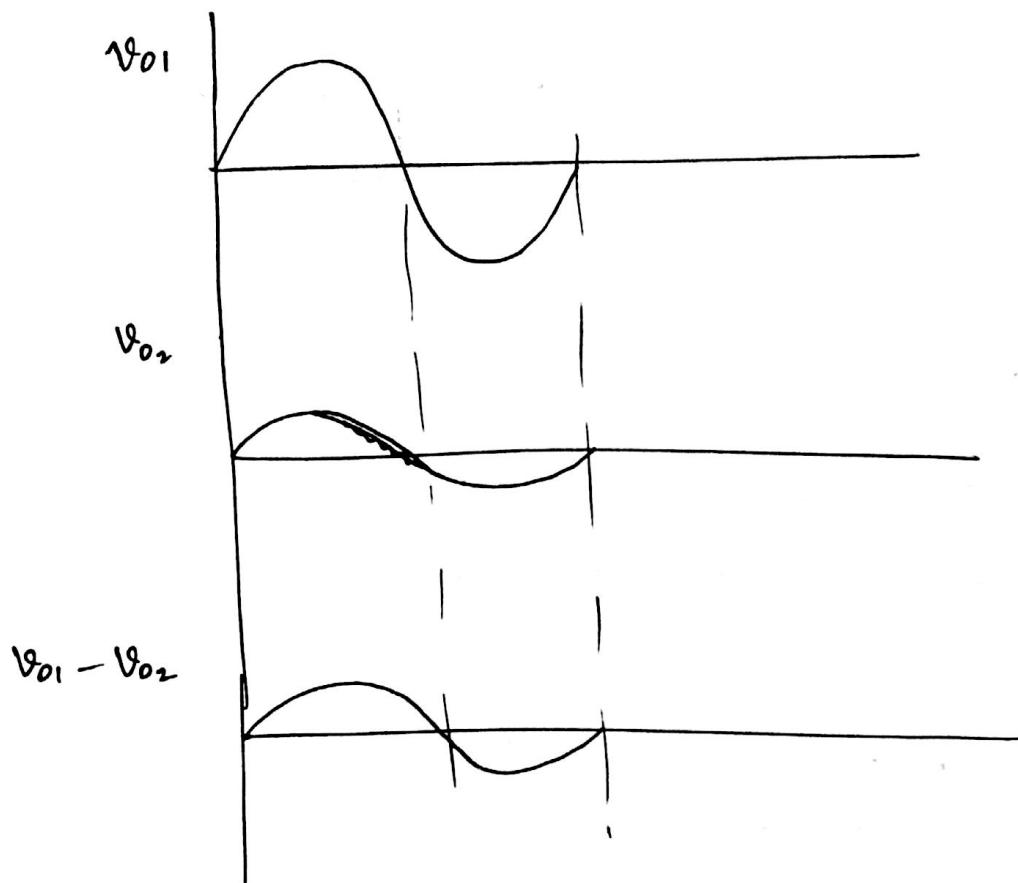

$$I_1 = \frac{V_p}{R_1 + j\omega L_1}$$

$$V_{o1} = j\omega I_1 M_1$$

$$= j\omega \frac{V_p}{R_1 + j\omega L_1} \cdot M_1$$

$$V_{o2} = j\omega \frac{V_p}{R_1 + j\omega L_1} M_2 \quad \text{"Don't Think Just Do It"}$$

— MyC_opie

$$V_o = V_{o1} - V_{o2}$$

$$V_o = j \frac{V_p}{R_1 + j\omega L_1} w(M_1 - M_2)$$

L_1 : self self inductance of S_1
 M_1, M_2 : mutual inductance
 of S_1, S_2 wrt P
MyCopic



Here, we don't consider self inductances of S_1, S_2 since there is no current drawn from S_1 or S_2 . V_{o1}, V_{o2} are induced.

$$\Rightarrow V_o \propto (M_1 - M_2)$$

↑
due to movement of core.


There is negligible energy loss (if R_1 is small).

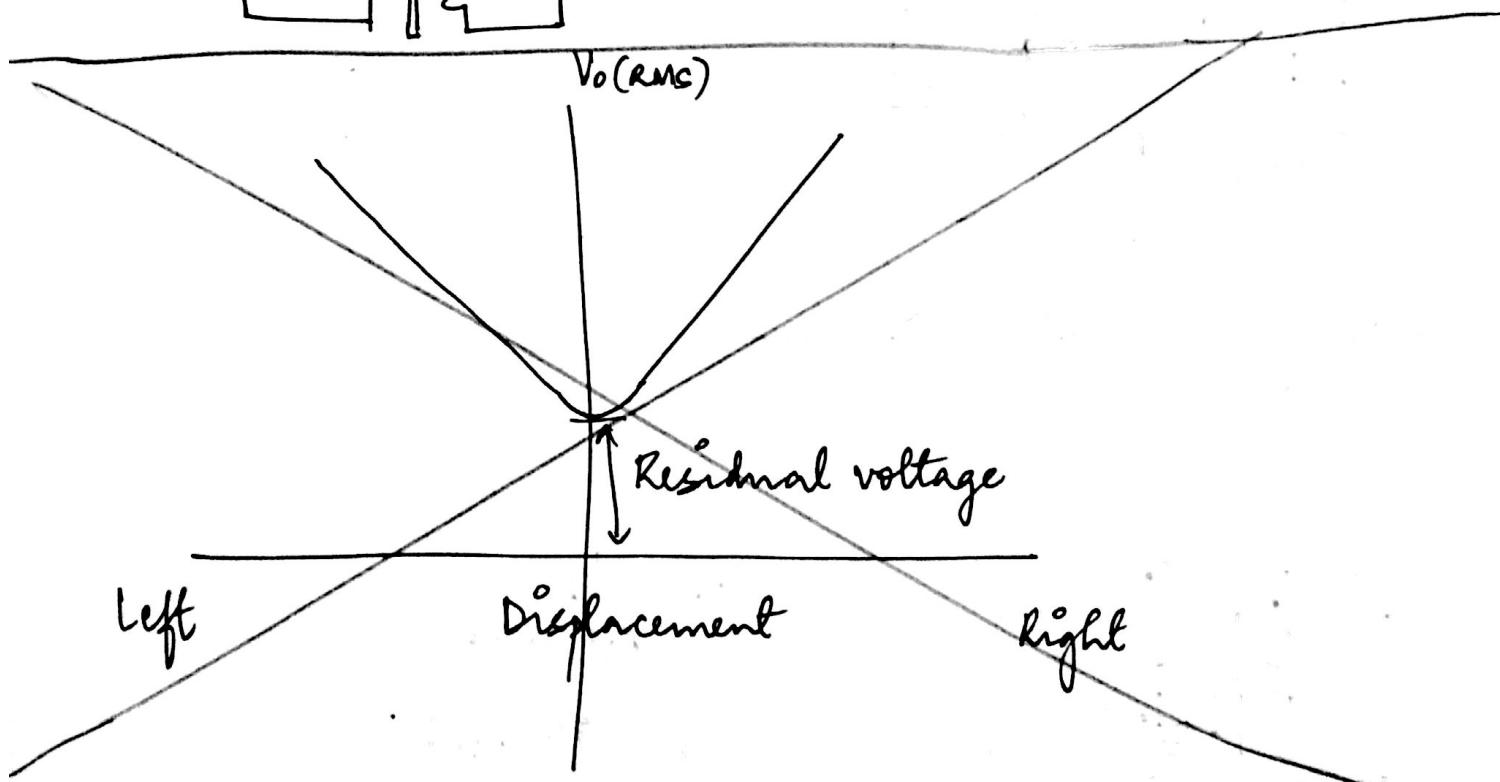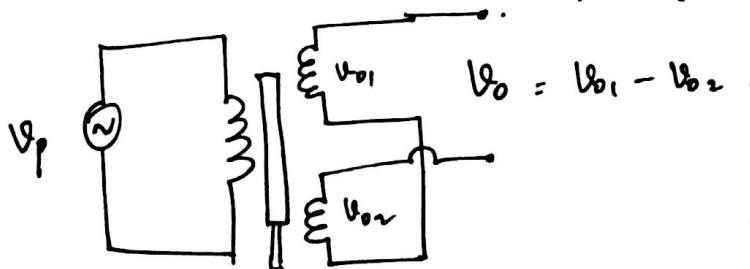Also, core can move more freely w/o friction.



Synchronous Machine

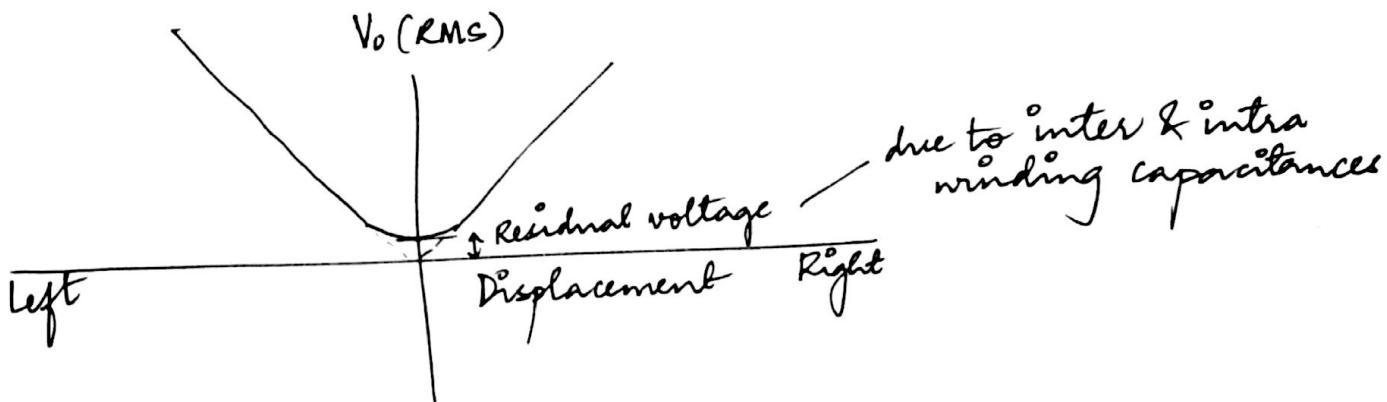- Can be used in
 1. Standalone operation
 2. Grid connected operation.
- A grid is a large electrical network consisting of various sources & loads.
- Interconnection b/w them consists of transmission & distribution systems
- Sources: Alternators. Renewable sources include wind, solar.



You can make this zero by having a lag-lead network




But, this balancing is for one particular frequency. There will be other harmonics for current thro S_1, S_2 .

Core can be laminated to reduce core loss.

The primary winding attracts core due to current thro it


Air - damping
Eddy current

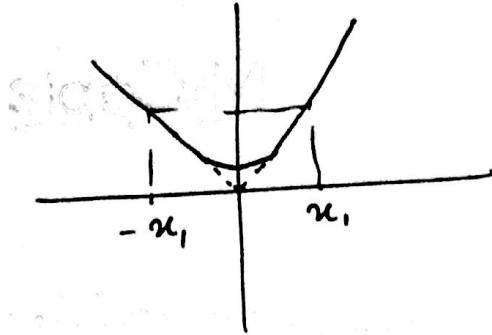Require extra force to be applied to move core.




At x , & $-x$, we get same output. How do we distinguish?


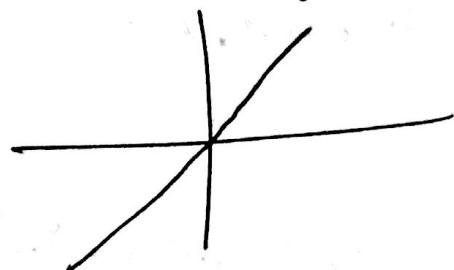
i.e.; how do we get characteristics of the form




Rectify V_{o1} as :

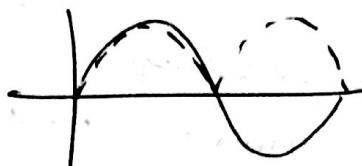

and V_{o2} as :

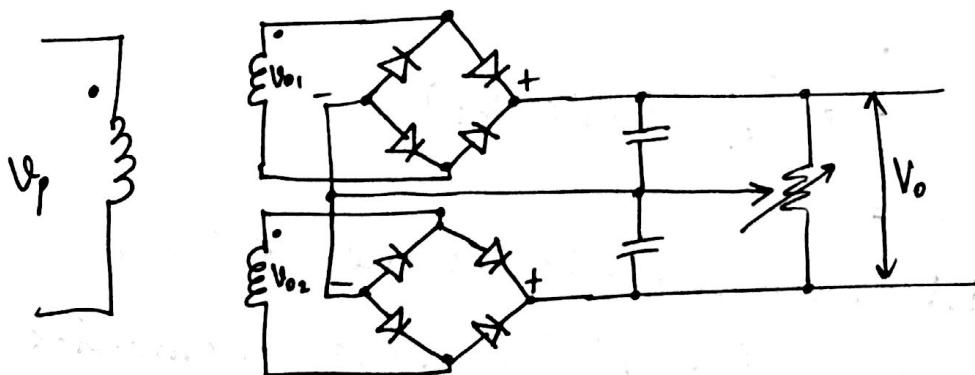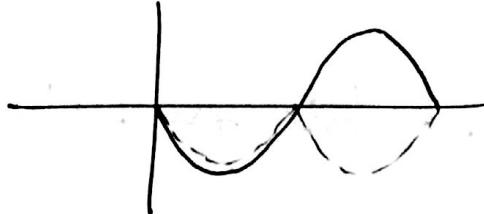

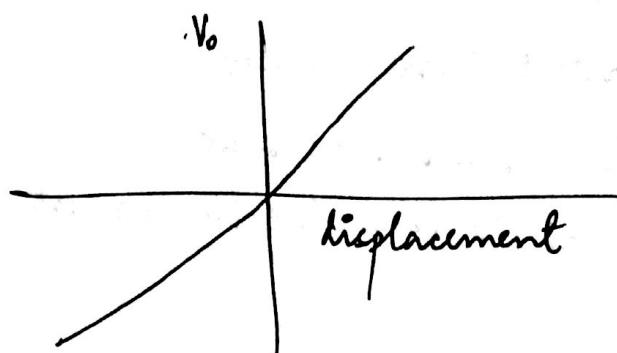So, whatever you're doing for S_1 ,
do the opposite
for S_2 .



But, diodes require turning on voltage.
As long as max amplitude
of $V_{o1}, V_{o2} > 0.7V$,
it's fine!